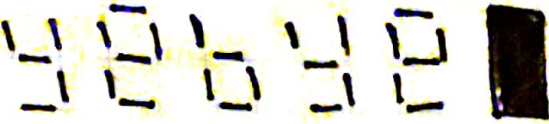
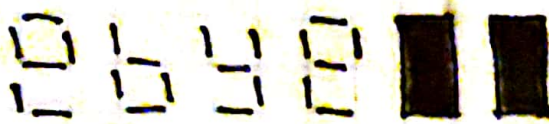

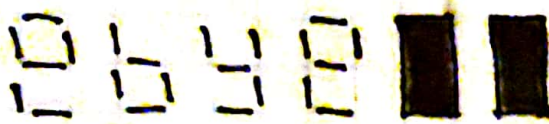






Verilog Scrolling Display "CPEN 842"

Cases


A:	█	█	█	█	█	█	M:	█	█	█	█	█	█	█	█
B:	█	█	█	█	█	█	N:	█	█	█	█	█	█	█	█
C:	█	█	█	█	█	█	O:	█	█	█	█	█	█	█	█
D:	█	█	█	█	█	█	P:	█	█	█	█	█	█	█	█
E:	█	█	█	█	█	█	Q:	█	█	█	█	█	█	█	█
F:	█	█	█	█	█	█	R:	█	█	█	█	█	█	█	█
G:	█	█	█	█	█	█	S:	█	█	█	█	█	█	█	█
H:	█	█	█	█	█	█	T:	█	█	█	█	█	█	█	█
I:	█	█	█	█	█	█	U:	█	█	█	█	█	█	█	█
J:	█	█	█	█	█	█	V:	█	█	█	█	█	█	█	█
K:	█	█	█	█	█	█	W:	█	█	█	█	█	█	█	█
L:	█	█	█	█	█	█	X:	█	█	█	█	█	█	█	█


incremented count = loop count + 1


y:   
 H:  
 p: 


b:  
 c: 


Encoding


 $\Rightarrow 7/b0000110$


 $\Rightarrow 7/b0000100$

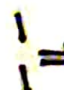 $\Rightarrow 7/b0000100$


 $\Rightarrow 7/b0000100$


 $\Rightarrow 7/b1111111$

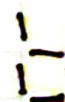 $\Rightarrow 7/b0000011$


 $\Rightarrow 7/b0000110$

 $\Rightarrow 7/b0000100$


 $\Rightarrow 7/b0000011$

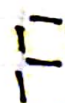 $\Rightarrow 7/b0000011$

Circuit Diagram

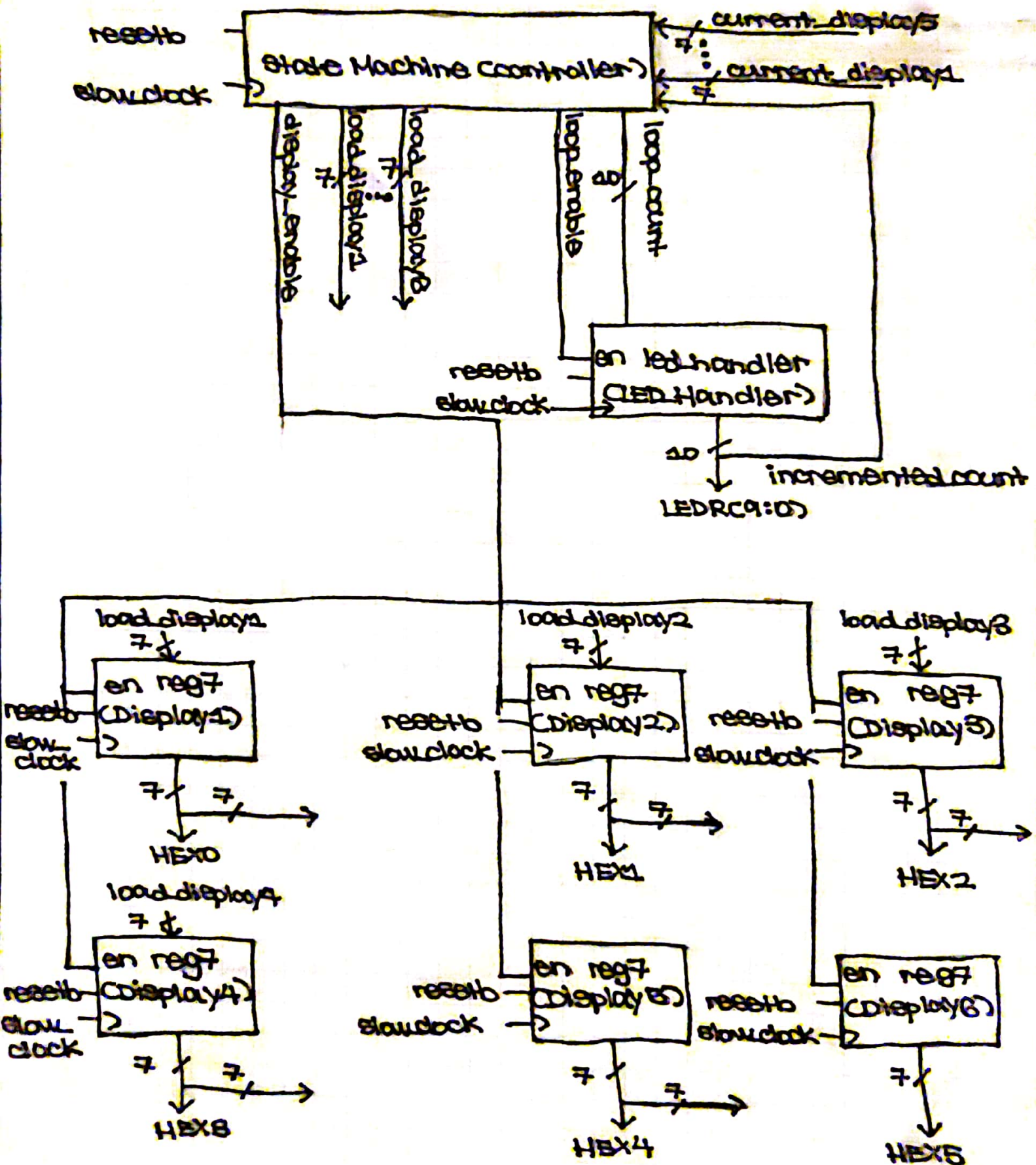

State Machine

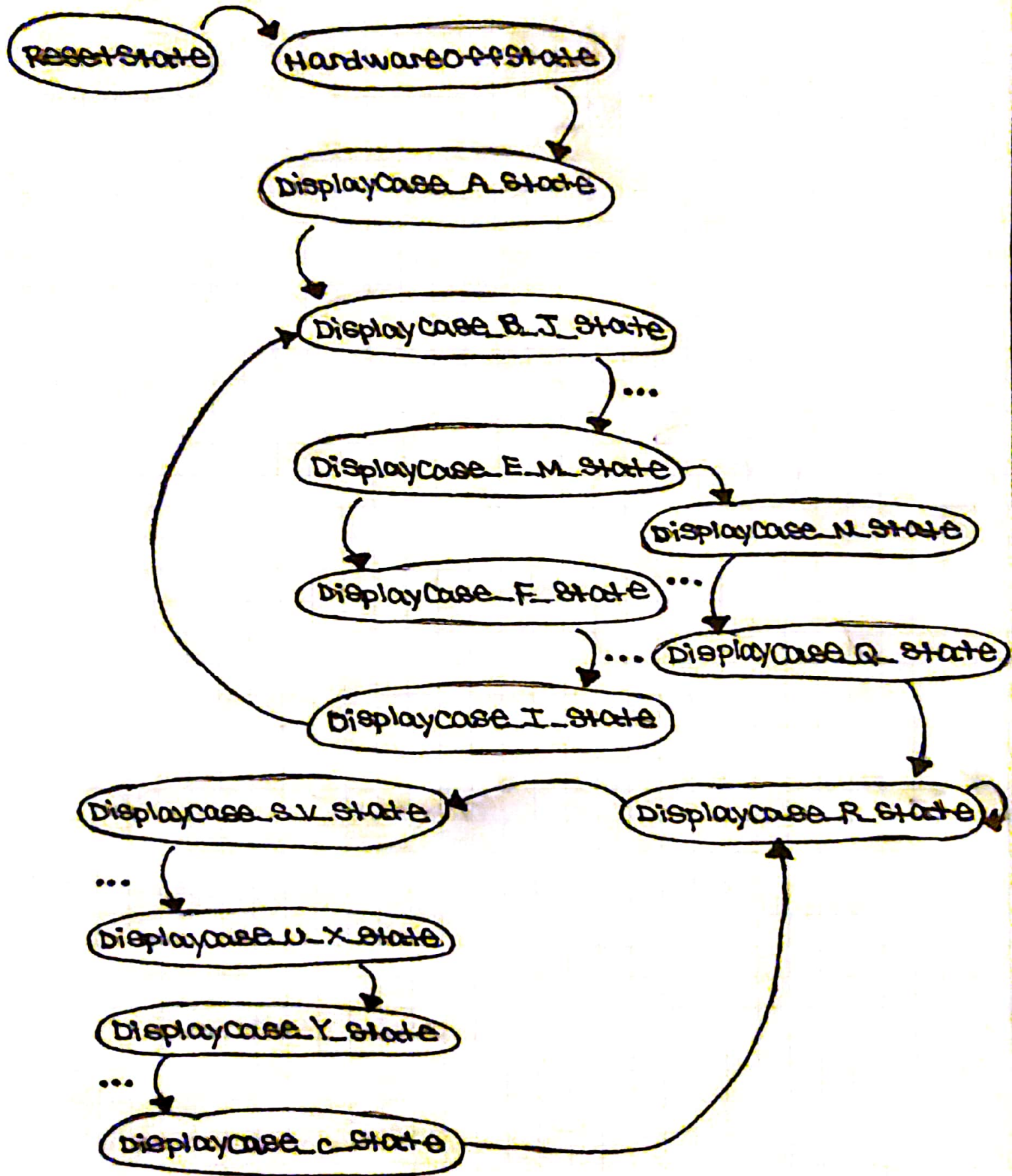

State Transitions

X \rightarrow ResetState: Cresetb == 0) ࣘ ࣘ (posedge clock)

ResetState \rightarrow HardwareOffState: Cresetb == 1) ࣘ ࣘ (posedge clock)

HardwareOffState \rightarrow DisplayCase_A_State:
Cresetb == 1) ࣘ ࣘ (posedge clock)

DisplayCase_A_State \rightarrow DisplayCase_B_I_State:
Cresetb == 1) ࣘ ࣘ (posedge clock)

DisplayCase_B_I_State \rightarrow DisplayCase_E_M_State:
Cresetb == 1) ࣘ ࣘ (posedge clock)

DisplayCase_E_M_State \rightarrow DisplayCase_F_State:
Cresetb == 1) ࣘ ࣘ (posedge clock)
ࣘ ࣘ Cincremented count < 10'b1000000000)

DisplayCase_E_M_State \rightarrow DisplayCase_N_State:
Cresetb == 1) ࣘ ࣘ (posedge clock)
ࣘ ࣘ Cincremented count == 10'b1000000000)

DisplayCase_F_State \rightarrow DisplayCase_I_State:
Cresetb == 1) ࣘ ࣘ (posedge clock)

DisplayCase_I_State \rightarrow DisplayCase_B_I_State:
Cresetb == 1) ࣘ ࣘ (posedge clock)

DisplayCase_N_State \rightarrow DisplayCase_Q_State:
Cresetb == 1) ࣘ ࣘ (posedge clock)

DisplayCase_Q_State \rightarrow DisplayCase_R_State:
Cresetb == 1) ࣘ ࣘ (posedge clock)

DisplayCase_R_State \rightarrow DisplayCase_S_V_State:
Cresetb == 1) ࣘ ࣘ (posedge clock)
ࣘ ࣘ Cincremented count != 10'b1111111111)

Displaycase_R_State → Displaycase_R_State:

(resetb == 1) && (posedge clock)

&& Cincrementedcount == 10'b1111111111)

Displaycase_R_State → Displaycase_U_X_State:

(resetb == 1) && (posedge clock)

Displaycase_U_X_State → Displaycase_Y_State:

(resetb == 1) && (posedge clock)

Displaycase_Y_State → Displaycase_C_State:

(resetb == 1) && (posedge clock)

Displaycase_C_State → Displaycase_R_State:

(resetb == 1) && (posedge clock)